

# ID Resources: Topic 5– Current and Resistance

1. In a certain circuit, the current as a function of time is given as:

$$i(t) = 3t^2 - 2t$$

where  $i$  is measured in milliamps and  $t$  is measured in seconds. How much charge passes through this circuit during the interval  $0 < t < 5.00 \text{ s}$ ?

- A. 28.0 mC
- B. 65.0 mC
- ✓ C. 100 mC
- D. 150 mC

2. Which of the following statements are true regarding current density?

- I. It is the current flowing per unit area
- II. It is a vector quantity with a direction opposite to that of the negative charges
- III. Its SI unit is  $\text{Am}^{-1}$

- A. I only
- B. II only
- C. I and II only
- ✓ D. I, II and III

3. A conductor carries a current of  $50 \mu\text{A}$ . If the area of cross-section of the conductor is  $50 \text{ mm}^2$ , then value of the current density is \_\_\_\_.

- ✓ A.  $10^{-6} \text{ Am}^{-2}$
- B.  $10^{-3} \text{ Am}^{-2}$
- C.  $0.5 \text{ Am}^{-2}$
- D.  $1.0 \text{ Am}^{-2}$

4. Ohm's Law states that the potential difference across a device is equal to \_\_\_\_.

- ✓ A. the current flowing through the device times the resistance of the device
- B. the current flowing through the device divided by the resistance of the device
- C. the resistance of the device divided by the current flowing through the device
- D. the current flowing through the device times the cross-sectional area of the device

5. Which of the following are the correct units for conductance and conductivity?

	Conductance	Conductivity
✓ A.	Siemens (S)	$(\Omega\text{m})^{-1}$
B.	Ohms ( $\Omega$ )	$\Omega\text{m}$
C.	$\Omega\text{m}$	Ohms ( $\Omega$ )
D.	$(\Omega\text{m})^{-1}$	Siemens (S)

6. A potential difference of  $2.0 \text{ V}$  is applied across a wire of cross sectional area  $2.5 \text{ mm}^2$ . The current which passes through the wire is  $3.2 \times 10^{-3} \text{ A}$ . What is the resistance of the wire?

- A.  $2.8 \times 10^2 \Omega$
- B.  $3.6 \times 10^2 \Omega$
- C.  $4.2 \times 10^2 \Omega$
- ✓ D.  $6.3 \times 10^2 \Omega$

7. Two cylindrical wires, 1 and 2, made of the same material, have the same resistance. If the length of wire 2 is twice that of wire 1, what is the ratio of their cross-sectional areas,  $A_1$  and  $A_2$ ?

- A.  $\frac{A_1}{A_2} = 2$
- B.  $\frac{A_1}{A_2} = 4$
- ✓ C.  $\frac{A_1}{A_2} = 0.5$
- D.  $\frac{A_1}{A_2} = 0.25$

8. Which of the following wires has the largest current flowing through it?

- A. a 1 m long copper wire of diameter 1 mm connected to a 10 V battery
- B. a 0.5 m long copper wire of diameter 0.5 mm connected to a 5 V battery
- ✓ C. a 2 m long copper wire of diameter 2 mm connected to a 20 V battery
- D. a 1 m long copper wire of diameter 0.5 mm connected to a 5 V battery

9. A particular wire has a diameter of 1.7 mm and length of 1.3 m. If its resistance is 15 m $\Omega$ , what is the resistivity of the metal from which it is made?

- A.  $1.0 \times 10^{-7} \Omega\text{m}$
- ✓ B.  $2.6 \times 10^{-8} \Omega\text{m}$
- C.  $4.4 \times 10^{-6} \Omega\text{m}$
- D.  $1.8 \times 10^{-5} \Omega\text{m}$


10. A 20 cm long and 1.0 mm diameter thick copper wire of resistivity  $1.7 \times 10^{-8} \Omega\text{m}$  is connected across a 3.0 V battery. The current through the wire is \_\_\_\_.

- A. 7.00 A
- B. 125 A
- ✓ C. 693 A
- D. 789 A

11. A copper wire of diameter 2.0 mm carries 12 A of current for an electric stove. Assuming the resistivity of copper of  $1.7 \times 10^{-8} \Omega\text{m}$ , the power dissipated in 2.0 m length of the wire is \_\_\_\_.

- A. 0.72 W
- B. 0.98 W
- C. 1.44 W
- ✓ D. 1.56 W

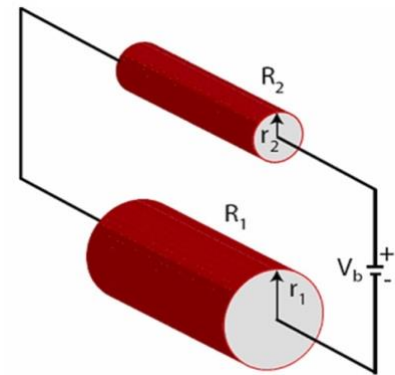12. Two cylinders are made out of the same material and are of equal length as shown. The cylinders are connected to a battery with voltage  $V_b$ . If the voltage drop across resistor  $R_2$  is  $0.810 \times V_b$ , what is the ratio of the radii  $r_1/r_2$  of the two cylinders?



- A. 1.10
- B. 1.51
- ✓ C. 2.06
- D. 3.31

13. The emf (electromotive force) is an \_\_\_\_.

- A. electric force vector
- B. electric field vector
- ✓ C. electric potential produced by a source
- D. electric current

14. A resistor with  $R = 10.0 \, \Omega$  is connected across a source of emf with potential difference  $V_{\text{emf}} = 1.50 \, \text{V}$ . What is the current flowing through the circuit?

- ✓ A. 0.15 A
- B. 0.23 A
- C. 6.67 A
- D. 150 A

15.  $N$  identical resistors are connected in series. The resistance of one of them is equal to  $R$ . What is the equivalent resistance of all  $N$  resistors?

- A.  $R/N$
- B.  $N/R$
- C.  $R$
- ✓ D.  $NR$

16. You make a series combination using a resistor A having a very large resistance and a resistor B having a very small resistance. The equivalent resistance of this combination will be


- ✓ A. slightly greater than the resistance of the resistor A
- B. slightly less than the resistance of the resistor A
- C. slightly greater than the resistance of the resistor B
- D. slightly less than the resistance of the resistor B

17. In the diagram below the current in the  $3.0 \, \Omega$  resistor is  $4.0 \, \text{A}$ . The potential difference between points A and B must be \_\_\_\_.




- A. 0.80 V
- B. 1.25 V
- C. 12 V
- ✓ D. 20 V

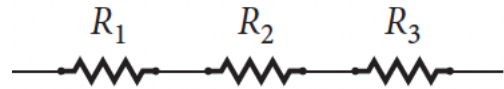18. Three identical resistors,  $R_1$ ,  $R_2$ , and  $R_3$ , are wired together as shown in the figure. An electric current is flowing through the three resistors. The current through  $R_2$  \_\_\_\_.



- ✓ A. is the same as the current through  $R_1$  and  $R_3$
- B. is a third of the current through  $R_1$  and  $R_3$
- C. is twice the sum of the current through  $R_1$  and  $R_3$
- D. is three times the current through  $R_1$  and  $R_3$

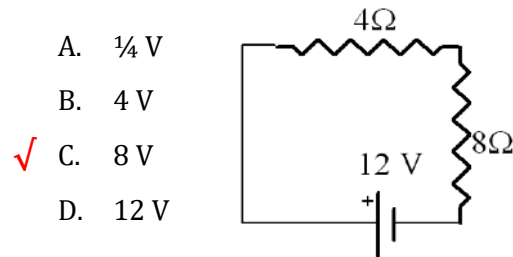19. What is voltage across the  $8 \, \Omega$  resistor?



- A.  $\frac{1}{4} \, \text{V}$
- B. 4 V
- ✓ C. 8 V
- D. 12 V

20. A battery has an unloaded terminal voltage of 48 V. When a load of  $15 \, \Omega$  is connected to the battery, the terminal voltage drops to 45.4 V. What is the internal resistance of the battery?

- ✓ A.  $0.86 \, \Omega$
- B.  $1.0 \, \Omega$
- C.  $1.2 \, \Omega$
- D.  $1.3 \, \Omega$

21. A battery has an internal resistance of  $1.3 \, \Omega$  and a voltage of 48 V. What is the load resistance which causes the voltage to drop to 45.4 V?

- A.  $0.587 \, \Omega$
- B.  $1.37 \, \Omega$
- C.  $2.63 \, \Omega$
- ✓ D.  $22.7 \, \Omega$


22. A battery has an internal resistance of  $1.3\ \Omega$  and a voltage of  $48.0\ \text{V}$ . If a load of  $15.0\ \Omega$  is connected to the battery, what is the voltage across the terminals of the battery?

- A.  $39.6\ \text{V}$
- ✓ B.  $44.2\ \text{V}$
- C.  $45.4\ \text{V}$
- D.  $48.0\ \text{V}$

23.  $N$  identical resistors are connected in parallel. The resistance of one of them is equal to  $R$ . What is the equivalent resistance of all  $N$  resistors?

- ✓ A.  $R/N$
- B.  $N/R$
- C.  $R$
- D.  $NR$

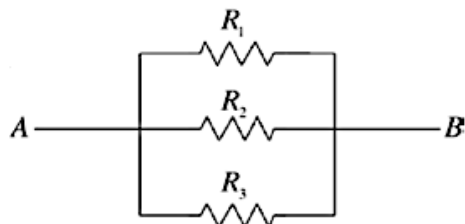24. What is the equivalent resistance of the circuit shown if  $R_1 = 24\ \Omega$ ,  $R_2 = 40\ \Omega$ ,  $R_3 = 16\ \Omega$ ?



- ✓ A.  $7.7\ \Omega$
- B.  $10\ \Omega$
- C.  $56\ \Omega$
- D.  $61\ \Omega$

25. You make a parallel combination using a resistor A having a very large resistance and a resistor B having a very small resistance. The equivalent resistance of this combination will be


- A. slightly greater than the resistance of the resistor A
- B. slightly less than the resistance of the resistor A
- C. slightly greater than the resistance of the resistor B
- ✓ D. slightly less than the resistance of the resistor B

26. Two identical light bulbs are connected to a battery. Will the light bulbs be brighter if they are connected to the battery in series or in parallel?

- A. in series
- ✓ B. in parallel
- C. The brightness will be the same in series and in parallel
- D. There is not enough information to determine an answer
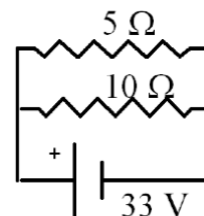
### Questions 27 to 29

Two resistors are connected to a battery as shown in the figure below.



27. What is the current in the  $5\ \Omega$  resistor?

- A.  $2.2\ \text{A}$
- B.  $3.3\ \text{A}$
- ✓ C.  $6.6\ \text{A}$
- D.  $9.9\ \text{A}$

28. What is the current in the  $10\ \Omega$  resistor?


- A.  $2.2\ \text{A}$
- ✓ B.  $3.3\ \text{A}$
- C.  $6.6\ \text{A}$
- D.  $9.9\ \text{A}$

29. What is the current supplied by the battery?


- A.  $2.2\ \text{A}$
- B.  $3.3\ \text{A}$
- C.  $6.6\ \text{A}$
- ✓ D.  $9.9\ \text{A}$

30. What is the total power dissipated in both resistors?

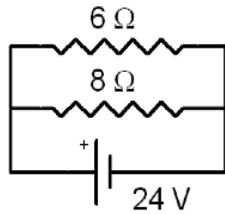- A. 0.68 W
- B. 5.2 W
- C. 12.3 W
- ✓ D. 168 W




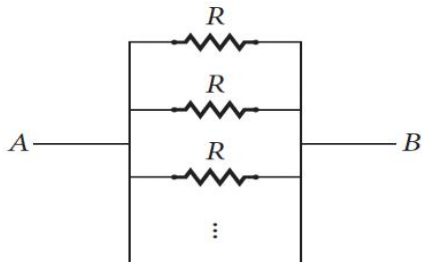31. As more identical resistors,  $R$ , are added to the circuit shown in the figure, the resistance between points A and B will \_\_\_\_.




- A. increase
- ✓ B. decrease
- C. stay the same
- D. Change in an unpredictable manner

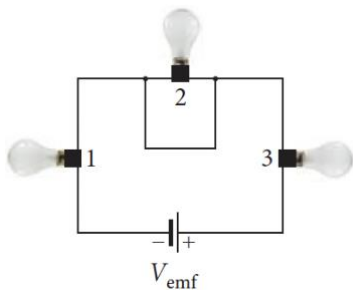32. Three light bulbs are connected in series with a battery that delivers a constant potential difference,  $V_{\text{emf}}$ . When a wire is connected across light bulb 2 as shown in the figure, light bulbs 1 and 3 \_\_\_\_.




- A. burn just as brightly as they did before the wire was connected.
- ✓ B. burn more brightly than they did before the wire was connected
- C. burn less brightly than they did before the wire was connected
- D. go out

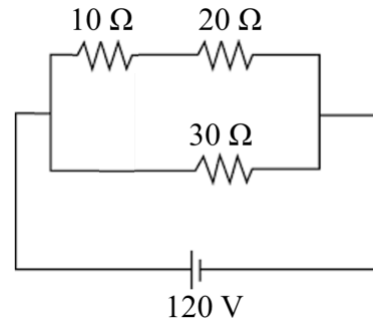33. A 10 ohm resistor is attached to a 20 ohm resistor in series. This combination is then attached to a 30 ohm resistor in parallel. This is then connected to a 120 V battery. What is the current flow through the 20 ohm resistor?




- ✓ A. 4.0 A
- B. 6.0 A
- C. 8.0 A
- D. 16 A

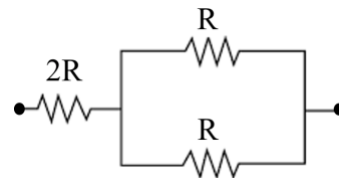34. Two resistors of resistance  $R$  are connected in parallel. The combination is connected in series to a resistor of resistance  $2R$ . What is the resistance of this combination of resistors?




- A. 0.5 R
- B. R
- C. 1.0 R
- ✓ D. 2.5 R

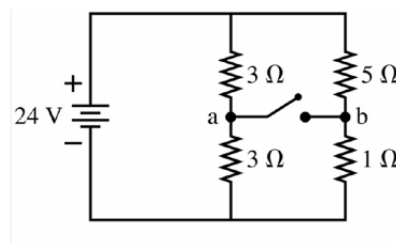35. What is the battery current  $I_{\text{bat}}$  when the switch in the figure is closed?




- A. 1.09 A
- B. 8.00 A
- ✓ C. 9.14 A
- D. 12.5 A

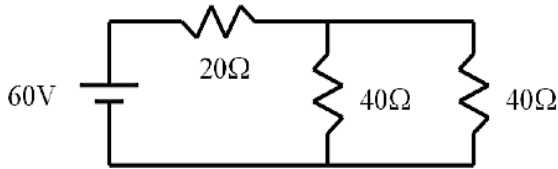36. What is the current in the  $20\ \Omega$  resistor in the circuit in the figure?




- A. 0.33 A
- B. 0.60 A
- C. 1.0 A
- ✓ D. 1.5 A

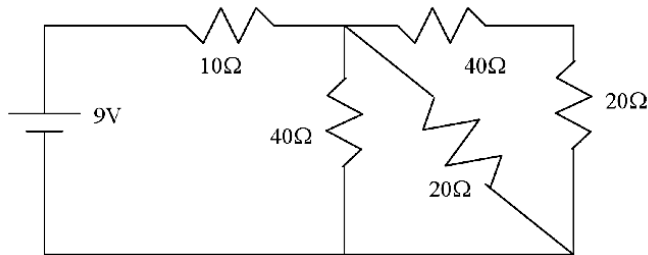37. What is the current that flows out of the ideal 9.0 V battery in the circuit in the figure?




- A. 0.07 A
- ✓ B. 0.43 A
- C. 0.54 A
- D. 0.90 A

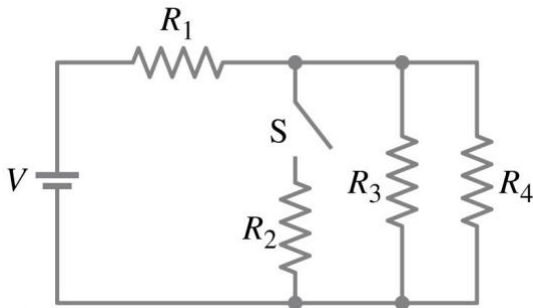38. What happens to the voltage across the resistor  $R_4$  when the switch is closed?




- A. Increases
- ✓ B. Decreases
- C. Stays the same
- D. Increases and then decreases

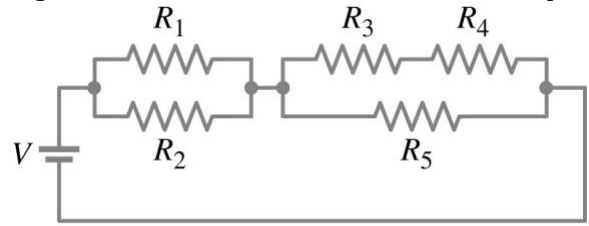39. Which resistor has the greatest current going through it? Assume that all the resistors are equal.




- A.  $R_1$
- ✓ B.  $R_5$
- C.  $R_3$  and  $R_4$
- D.  $R_1$  and  $R_2$

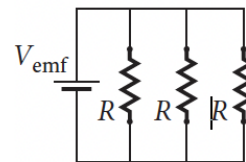
40. Which combination of resistors has the highest equivalent resistance?




(a)

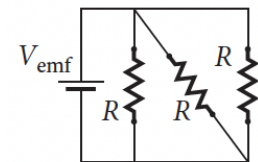

(b)

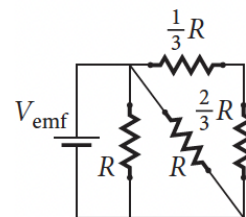

(c)

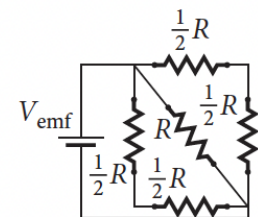


(d)

- ✓ A. Combination (a)
- B. Combination (b)
- C. Combination (c)
- D. Combination (d)
- E. The equivalent resistance is the same for all the four circuits

41. How much energy is used by a 15 W electric motor if it operates for half an hour?

- A. 127 J
- B. 450 J
- C. 9000 J
- ✓ D. 27000 J

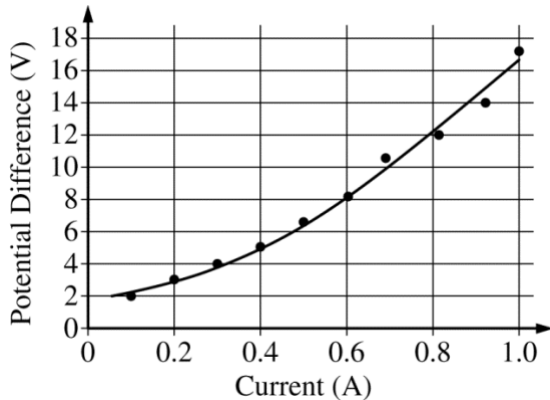42. The graph below shows experimental data for the potential difference across a lightbulb as a function of the current through the light bulb. The power dissipated by the lightbulb when the potential difference across the bulb is 12 V is most nearly \_\_\_\_.



- A. 0.067 W
- B. 7.7 W
- ✓ C. 9.6 W
- D. 12 W


43. If the current through a resistor is increased by a factor of 4, how does this affect the power dissipated?

- A. It decreases by a factor of 4
- B. It increases by a factor of 4
- C. It decreases by a factor of 8
- ✓ D. It increases by a factor of 16

44. If the electric [potential across a resistor is increased by a factor of 4, how does this affect the power dissipated?

- A. It decreases by a factor of 4
- B. It increases by a factor of 4
- C. It decreases by a factor of 8
- ✓ D. It increases by a factor of 16

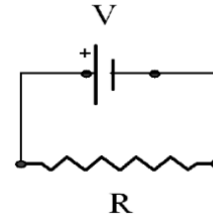45. In order to double the power dissipated in the resistor R, \_\_\_\_.



- A. double the resistance R
- B. double the voltage V
- ✓ C. increase the voltage V by about 40%.
- D. decrease the resistance R by a factor of four

46. Two lightbulbs operate at 120 V, but one has a power rating of 25 W while the other has a power rating of 100 W. Which one has the greater resistance?

- A. The 25 W bulb
- ✓ B. The 100 W bulb
- C. Both have the same resistance
- D. Resistance is independent of power


47. A fixed voltage is applied across the length of a tungsten wire. An increase in the power dissipated by the wire would result if which of the following could be increased?

- A. The resistivity of the tungsten
- ✓ B. The cross-sectional area of the wire
- C. The length of the wire
- D. The temperature of the wire

48. Copper wire A has twice the length and half the diameter of copper wire B, but carries the same current  $I$ . If  $P$  is the rate at which energy is dissipated in wire B, what is the rate at which energy is dissipated in wire A?

- A.  $P/8$
- B.  $P/4$
- C.  $4P$
- ✓ D.  $8P$

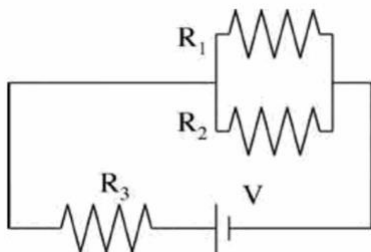49. In the circuit shown,  $R_1 = 9.00 \, \Omega$ ,  $R_2 = 14.0 \, \Omega$ ,  $R_3 = 2.50 \, \Omega$ , and  $V = 16.0 \, V$ . Find the total power dissipated in the circuit in  $W$ .



- A. 2.00 W
- B. 10.1 W
- C. 22.1 W
- ✓ D. 32.1 W

50. A 12.0 V battery is connected to a 7.54 ohm resistor and a current of 0.999A is measured to flow through the resistor. How much power is dissipated as heat inside the battery?

- ✓ A. 4.47 W
- B. 7.10 W
- C. 12.0 W
- D. 19.1 W

### Free Response:

1. True or False.

- a. Two wires made of different materials, but of same length and area of cross section, have the same resistivity. (False)
- b. Conductors of the same material with different geometries have different resistances. (True)
- c. Conductors of the same material with different geometries have the same resistivity. (True)
- d. The resistance of a copper wire of constant cross-sectional area is directly proportional to its length. (True)
- e. The resistance of a copper wire of constant length is directly proportional to its cross-sectional area. (False)

2. A copper wire 3.2 mm in diameter carries a 5.0 A current. Determine the current density in the wire.

$$j = \frac{I}{A} = \frac{I}{\pi r^2}$$

$$j = \frac{5.0 \, A}{\pi (1.6 \times 10^{-3} \, m)^2} = 6.2 \times 10^5 \, A m^{-2}$$

3. What is the resistance of a copper wire of length  $l = 10.9 \, m$  and diameter  $d = 1.30 \, mm$ ? The resistivity of copper is  $1.72 \times 10^{-8} \, \Omega m$ .

$$R = \frac{\rho L}{A} = (1.72 \times 10^{-8} \, \Omega m) \left( \frac{10.9 \, m}{\pi (0.65 \times 10^{-3} \, m)^2} \right) = 0.141 \, \Omega$$



4. A potential difference of 12.0 V is applied across a wire of cross-sectional area 4.50 mm<sup>2</sup> and length 1000 km. The current passing through the wire is  $3.20 \times 10^{-3}$  A.

- a. What is the resistance of the wire?

$$R = \frac{V}{I} = \frac{12.0 \text{ V}}{3.20 \times 10^{-3} \text{ A}} = 3750 \, \Omega$$

- b. What is the resistivity of the wire?

$$\rho = \frac{RA}{l} = \frac{(3750 \, \Omega)(4.50 \times 10^{-6} \text{ m}^2)}{1000 \, 000 \text{ m}} = 1.69 \times 10^{-8} \, \Omega\text{m}$$

- c. What is the conductivity of the wire?


$$\sigma = \frac{1}{\rho} = \frac{1}{1.69 \times 10^{-8} \, \Omega\text{m}} = 5.92 \times 10^7 (\Omega\text{m})^{-1}$$

5. Two conductors are made of the same material and have the same length  $L$ . Conductor A is a hollow tube with inside diameter 2.00 mm and outside diameter 3.00 mm; conductor B is a solid wire with radius  $R_B$ . What value of  $R_B$  is required for the two conductors to have the same resistance measured between their ends?

The resistance will be the same when their cross-sectional areas are the same.

$$\pi R_B^2 = \pi \left(\frac{d_o}{2}\right)^2 - \pi \left(\frac{d_i}{2}\right)^2 \Rightarrow R_B = \frac{1}{2} \sqrt{d_o^2 - d_i^2}$$
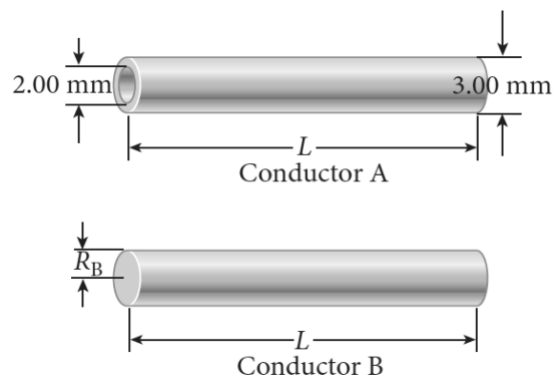
$$R_B = \frac{1}{2} \sqrt{(3.00 \text{ mm})^2 - (2.00 \text{ mm})^2} = 1.12 \text{ mm}$$




6. A potential difference of 12.0 V is applied across a wire of cross-sectional area 4.50 mm<sup>2</sup> and length 1000 km. The current passing through the wire is  $3.20 \times 10^{-3}$  A.

- a. What is the resistance of the wire?

$$R = \frac{\Delta V}{I} = \frac{12.0 \text{ V}}{3.20 \times 10^{-3} \text{ A}} = 3750 \, \Omega$$

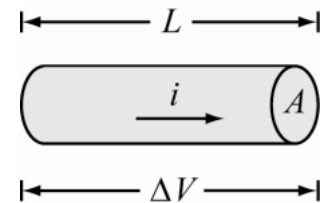- b. What is the resistivity of the wire?

$$\rho = \frac{RA}{l} = \frac{(3750 \, \Omega)(4.50 \times 10^{-6} \text{ m}^2)}{1000 \times 10^3 \text{ m}} = 1.69 \times 10^{-8} \, \Omega\text{m}$$



7. Consider a battery that has  $V_t = 15.0 \text{ V}$  when it is not connected to a circuit. When a  $10.0 \Omega$  resistor is connected with the battery, the potential difference across the battery's terminals drops to  $12.5 \text{ V}$ . What is the internal resistance of the battery?


The current flowing through the resistor:

$$I = \frac{V}{R} = \frac{12.5 \text{ V}}{10.0 \Omega} = 1.25 \text{ A}$$

$$V_t = IR_{eq} = I(R + R_i)$$

$$15.0 \text{ V} = (1.25 \text{ A})(10 \Omega + R_i)$$

$$R_i = 2.0 \Omega$$

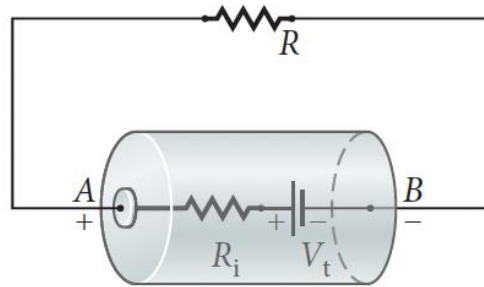

8. A battery with an emf of  $\mathcal{E} = 12.0 \text{ V}$  has a terminal voltage of  $11.5 \text{ V}$  when the current is  $I = 3.0 \text{ A}$ .

- a. Calculate the battery's internal resistance  $r$ .

$$\mathcal{E} = IR + Ir$$

$$12.0 \text{ V} = 11.5 \text{ V} + (3.0 \text{ A})r$$

$$r = \frac{0.5 \text{ V}}{3.0 \text{ A}} = 0.17 \Omega$$


- b. Find the load resistance  $R$ .

$$R = \frac{V}{I} = \frac{11.5 \text{ V}}{3.0 \text{ A}} = 3.8 \Omega$$

9. The figure shows a battery of emf  $\mathcal{E}$  and internal resistance  $r = 0.15 \Omega$  connected to an external resistor  $R = 8.00 \Omega$ .

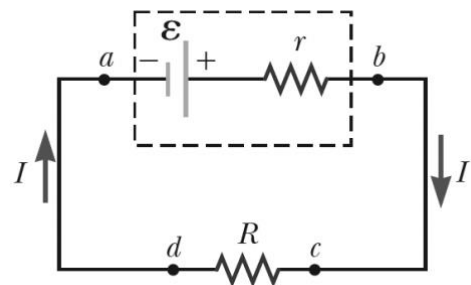- a. Find the current in an  $8.00 \Omega$  resistor if the voltage across the battery (the terminal voltage) is  $9.00 \text{ V}$ .

$$I = \frac{V}{R} = \frac{9.00 \text{ V}}{8.00 \Omega} = 1.13 \text{ A}$$



- b. What is the emf of the battery?

$$\mathcal{E} = IR + Ir$$

$$\mathcal{E} = 9.00 \text{ V} + (1.13 \text{ A})(0.15 \Omega)$$

$$\mathcal{E} = 9.17 \text{ V}$$

10. The figure below shows three resistors connected in a circuit.


- a. What is the equivalent resistance of the circuit?

The two  $20\ \Omega$  resistors are in parallel with each other.

$$\frac{1}{R_p} = \frac{1}{20\ \Omega} + \frac{1}{20\ \Omega} = \frac{1}{10\ \Omega}$$

$$R_p = 10\ \Omega$$
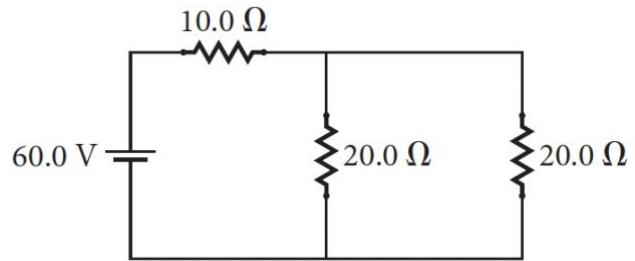
$$R_{eq} = 10\ \Omega + R_p = 10\ \Omega + 10\ \Omega = 20\ \Omega$$



- b. What is the current through the  $10\ \Omega$  resistor?

$$I = \frac{V}{R_{eq}} = \frac{60.0\ V}{20\ \Omega} = 3.0\ A$$

- c. What is the voltage across the  $20\ \Omega$  resistors?

$$V = IR_p = (3.0\ A)(10\ \Omega) = 30\ V$$


11. The figure below shows a circuit with four resistors.

- a. What is the equivalent resistance of the circuit when the switch is open?

$$R_{eq} = \left( \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4} \right)^{-1}$$

$$R_{eq} = \left( \frac{1}{3.00\ \Omega + 3.00\ \Omega} + \frac{1}{5.00\ \Omega + 1.00\ \Omega} \right)^{-1}$$

$$R_{eq} = 3.00\ \Omega$$

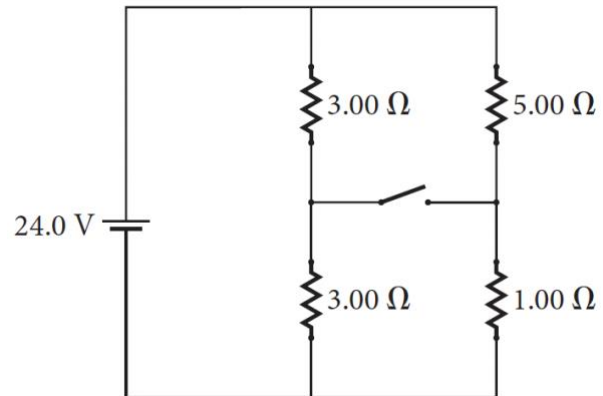

- b. What is the current in the circuit when the switch is open?

$$I = \frac{V}{R_{eq}} = \frac{24.0\ V}{3.00\ \Omega} = 8.00\ A$$

- c. What is the equivalent resistance of the circuit when the switch is closed?

$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_3} \right)^{-1} + \left( \frac{1}{R_2} + \frac{1}{R_4} \right)^{-1}$$


$$R_{eq} = \left( \frac{1}{3.00\ \Omega} + \frac{1}{5.00\ \Omega} \right)^{-1} + \left( \frac{1}{3.00\ \Omega} + \frac{1}{1.00\ \Omega} \right)^{-1}$$

$$R_{eq} = 1.88\ \Omega + 0.75\ \Omega = 2.63\ \Omega$$

- d. What is the current in the circuit when the switch is closed?

$$I = \frac{V}{R_{eq}} = \frac{24.0\ V}{2.63\ \Omega} = 9.14\ A$$

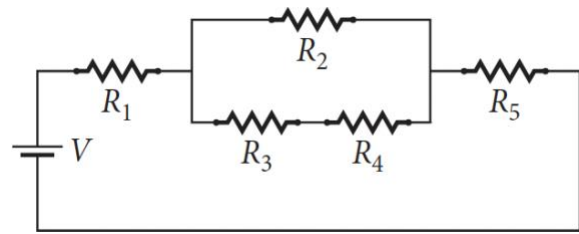12. For the circuit shown in the figure,  $R_1 = 6.00 \, \Omega$ ,  $R_2 = 6.00 \, \Omega$ ,  $R_3 = 2.00 \, \Omega$ ,  $R_4 = 4.00 \, \Omega$ ,  $R_5 = 3.00 \, \Omega$ , and the potential difference is 12.0 V.



- a. What is the equivalent resistance for the circuit?

$$R_{eq} = R_1 + \left( \frac{1}{R_2} + \frac{1}{R_3 + R_4} \right)^{-1} + R_5$$

$$R_{eq} = 6.00 \, \Omega + \left( \frac{1}{6.00 \, \Omega} + \frac{1}{2.00 \, \Omega + 4.00 \, \Omega} \right)^{-1} + 3.00 \, \Omega$$

$$R_{eq} = 6.00 \, \Omega + 3.00 \, \Omega + 3.00 \, \Omega = 12.0 \, \Omega$$

- b. What is the current through  $R_5$ ?


$$I = \frac{V}{R_{eq}} = \frac{12.0 \, \text{V}}{12.0 \, \Omega} = 1.00 \, \text{A}$$

- c. What is the potential drop across  $R_3$ ?

The current through each branch is  $I/2$ , so potential across  $R_3$ :

$$V_3 = \frac{IR_3}{2} = \frac{(1.00 \, \text{A})(2.00 \, \Omega)}{2} = 1.00 \, \text{V}$$

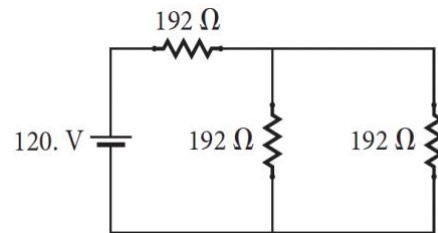13. Three resistors are connected across a battery as shown in the figure.



- a. What is the equivalent resistance of the circuit?

$$R_{eq} = 192 \, \Omega + \left( \frac{1}{192 \, \Omega} + \frac{1}{192 \, \Omega} \right)^{-1}$$

$$R_{eq} = 192 \, \Omega + 96 \, \Omega = 288 \, \Omega$$

- b. How much power is dissipated across the three resistors?

$$P = \frac{V^2}{R_{eq}} = \frac{(120 \, \text{V})^2}{288 \, \Omega} = 50 \, \text{W}$$

- c. Determine the potential drop across each resistor.

Current from the supply:

$$I = \frac{V}{R_{eq}} = \frac{120 \, \text{V}}{288 \, \Omega} = 0.417 \, \text{A}$$

$$V_1 = IR_1 = (0.417 \, \text{A})(192 \, \Omega) = 80 \, \text{V}$$

$$V_2 = V_3 = IR_p = (0.417 \, \text{A})(96 \, \Omega) = 40 \, \text{V}$$